

# Robust and Optimal Control

## A Two-port Framework Approach

# Linear Fractional Transformation

### Definition of a linear system

If  $f(x)$  is linear, then it satisfies


1. **homogenous**

$$f(ax) = af(x)$$

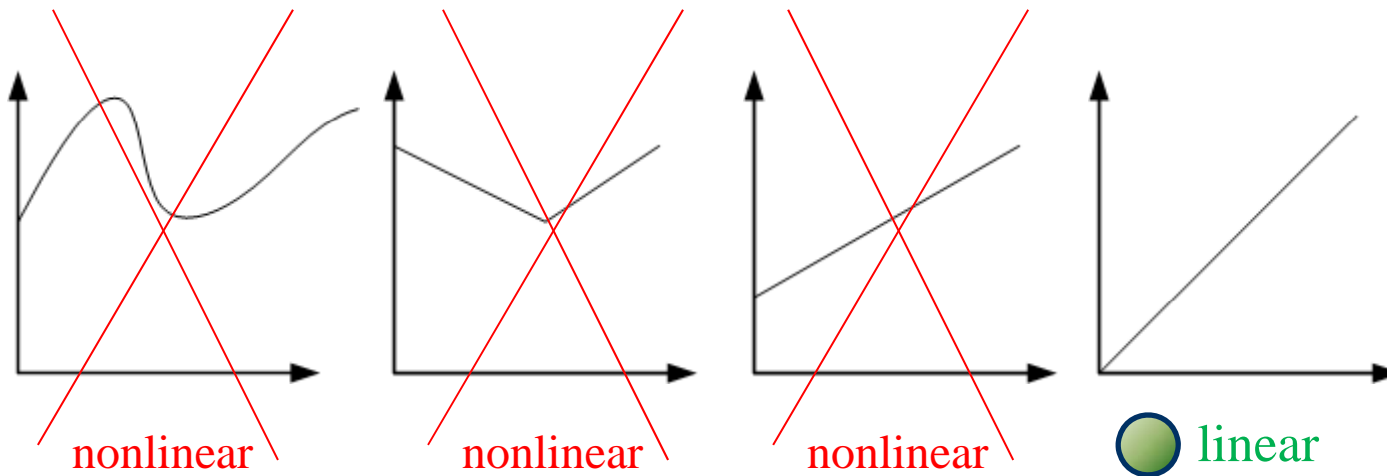2. **superposition**


$$f(x_1 + x_2) = f(x_1) + f(x_2) \text{ or}$$

$$f(a_1x_1 + a_2x_2) = a_1f(x_1) + a_2f(x_2)$$




**Transfer Function**

**Example: Determine the transfer function of the following circuit.**

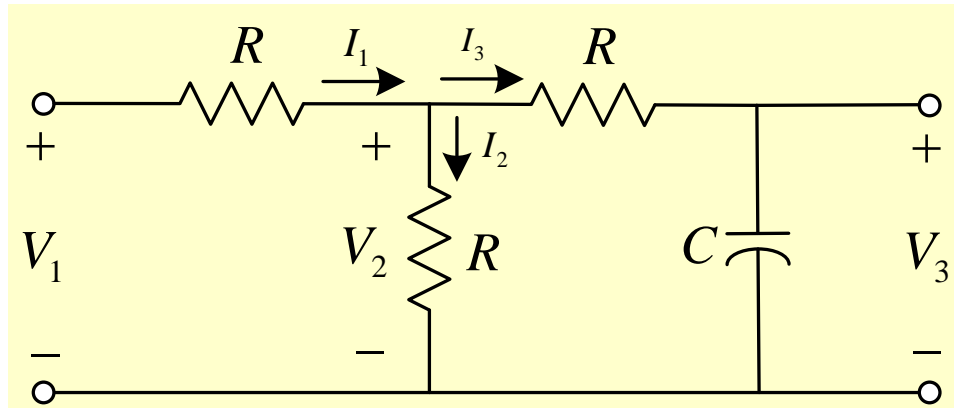

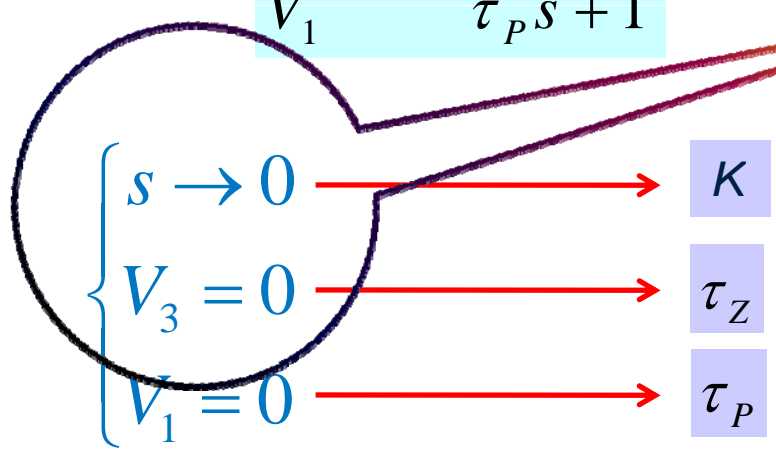**Method 1:** 
$$\frac{V_3}{V_1} = K \frac{\tau_Z s + 1}{\tau_P s + 1}$$



<Physical Insight>

- $s \rightarrow 0$ : the time goes to infinity
- $V_3 = 0$ : the short circuit in output
- $V_1 = 0$ : the short circuit in input

### Transfer Function

a) time goes to infinity  $s \rightarrow 0$ : dc gain

The capacitor is open circuit.  $\frac{V_3}{V_1} = \frac{R}{R+R} = \frac{1}{2}$


b)  $V_3 = 0$  the output is short circuit

$\tau_z$ : the time constant of the existing circuit

$$\tau_z = R_{eq} \times C_{eq} = 0 \times C_{eq} = 0$$

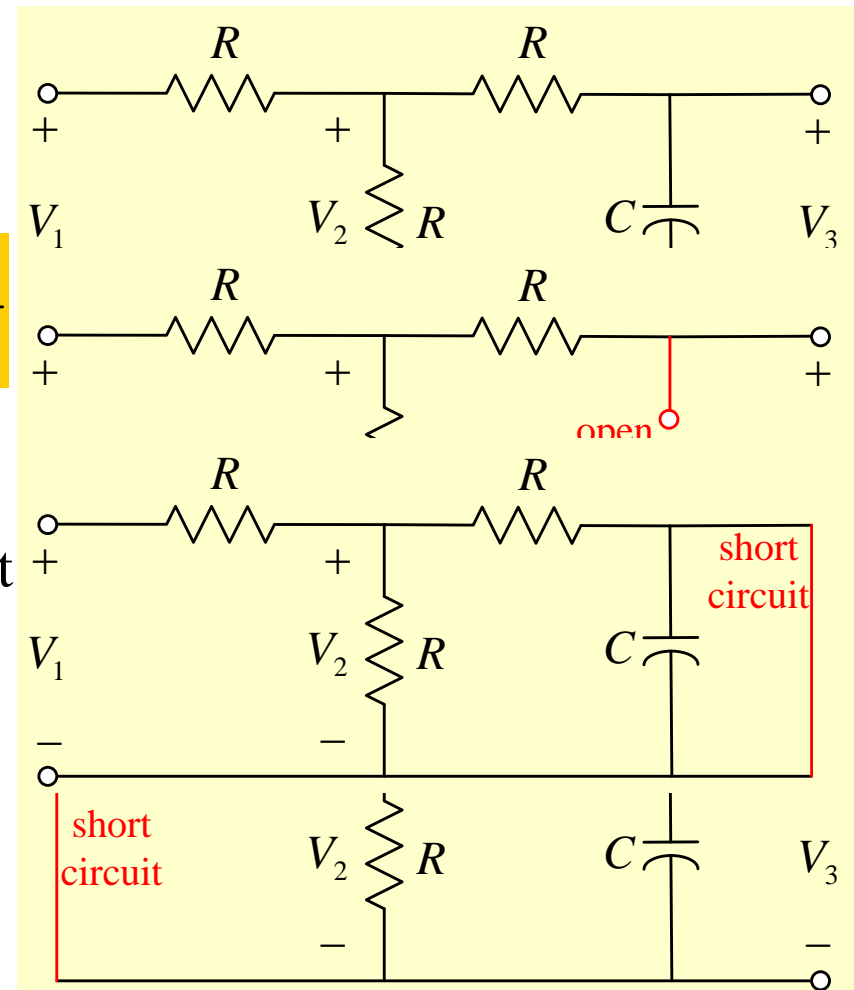
c)  $V_1 = 0$  the input is short circuit

$$\tau_p = R_{eq} \times C_{eq} = \frac{3}{2} R \times C$$



$$T(s) = \frac{1}{2} \frac{1}{\left(\frac{3RC}{2}\right)s + 1} = \frac{1}{3RCs + 2}$$

**Example:**

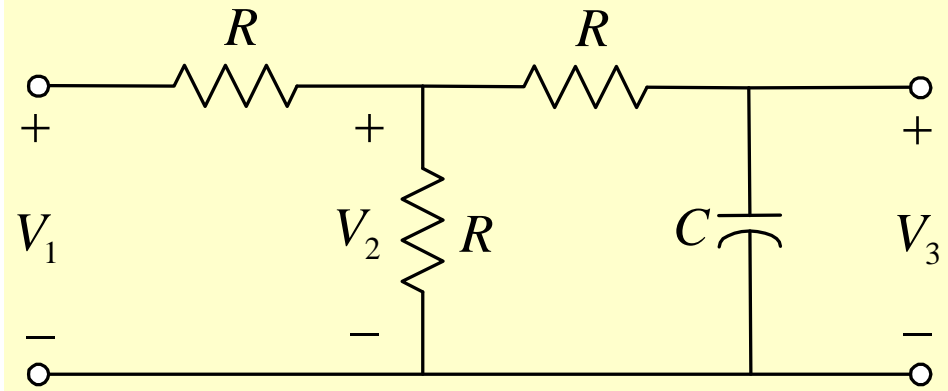

**Method 2: Mason's Rule**

$$M = \frac{\sum_j M_j \Delta_j}{\Delta}$$

$M$  = transfer function or gain of the system

$M_j$  = gain of one forward path

$j$  = an integer representing the forward paths in the system

$\Delta_j = 1 +$ the loops remaining after removing path  $j$ .

(1+the loops that don't touch the forward path  $M_j$ )

If none remain, then  $\Delta_j = 1$

$$\begin{aligned} \Delta = & 1 - \sum \text{loop gains} + \sum \text{nontouching loop gains taken two at a time} \\ & - \sum \text{nontouching loop gains taken three at a time} \\ & + \sum \text{nontouching loop gains taken four at a time} \dots \end{aligned}$$